

**Current Electricity**

**&**

**Ohm's Law**

# **Circuit Basics**

**All electrical circuits require three elements.**

**(1) A source voltage, that is, an electron pump usually a battery or power supply.**

**[ ENERGY IN ]**


**(2) A conductor to carry electrons from and to the voltage source (pump). The conductor is often a wire.**

**[ENERGY TRANSFER]**






**(3) A load or resistance. A point where energy is extracted form the circuit in the form of heat, light, motion, etc.**

**[ENERGY OUT]**


# THE MOST BASIC ELECTRICAL CIRCUIT

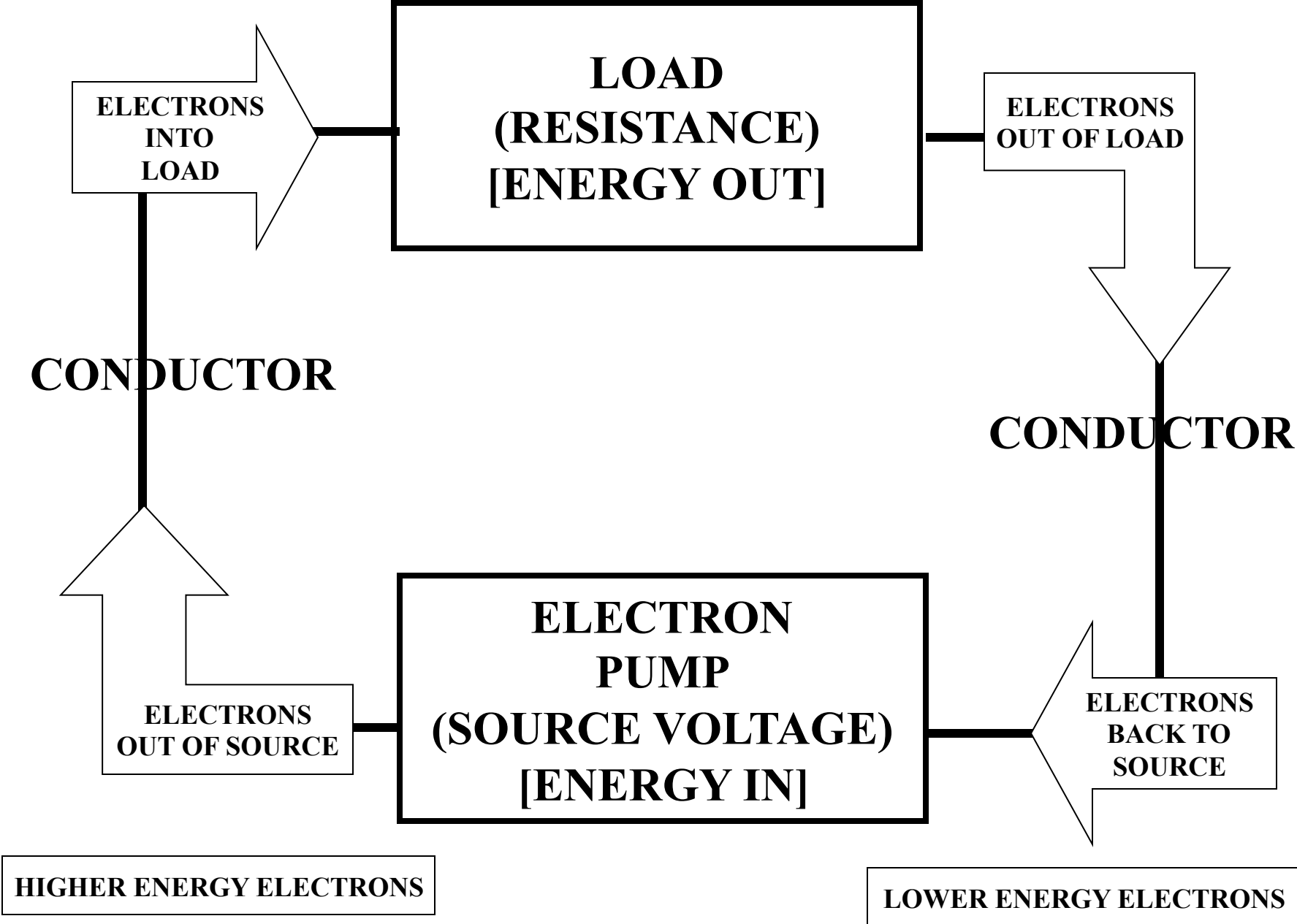

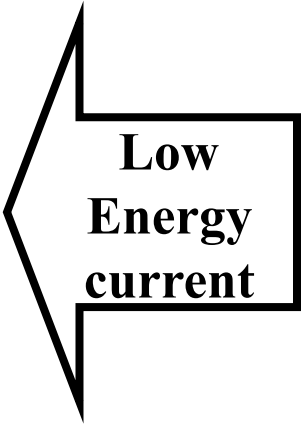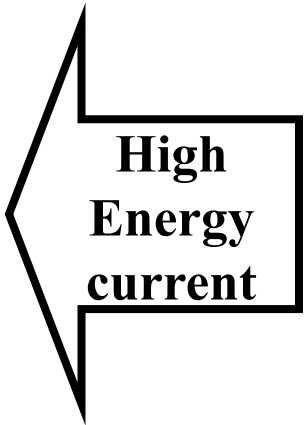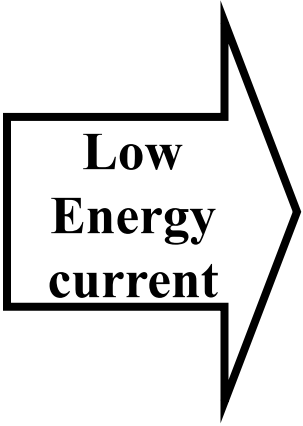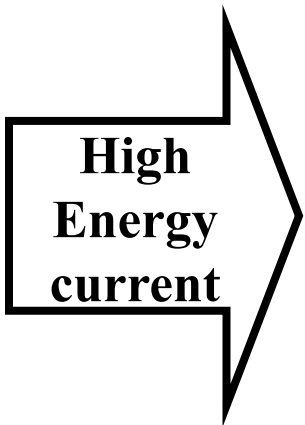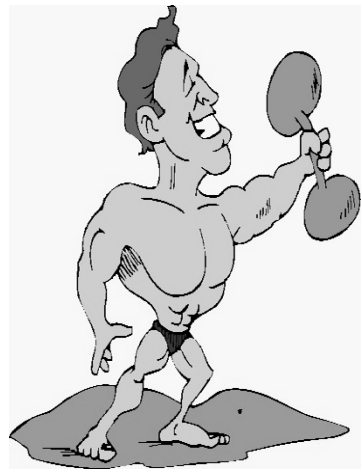
# Potential Changes of Current In a Circuit



# Potential Rise Across a Power Source

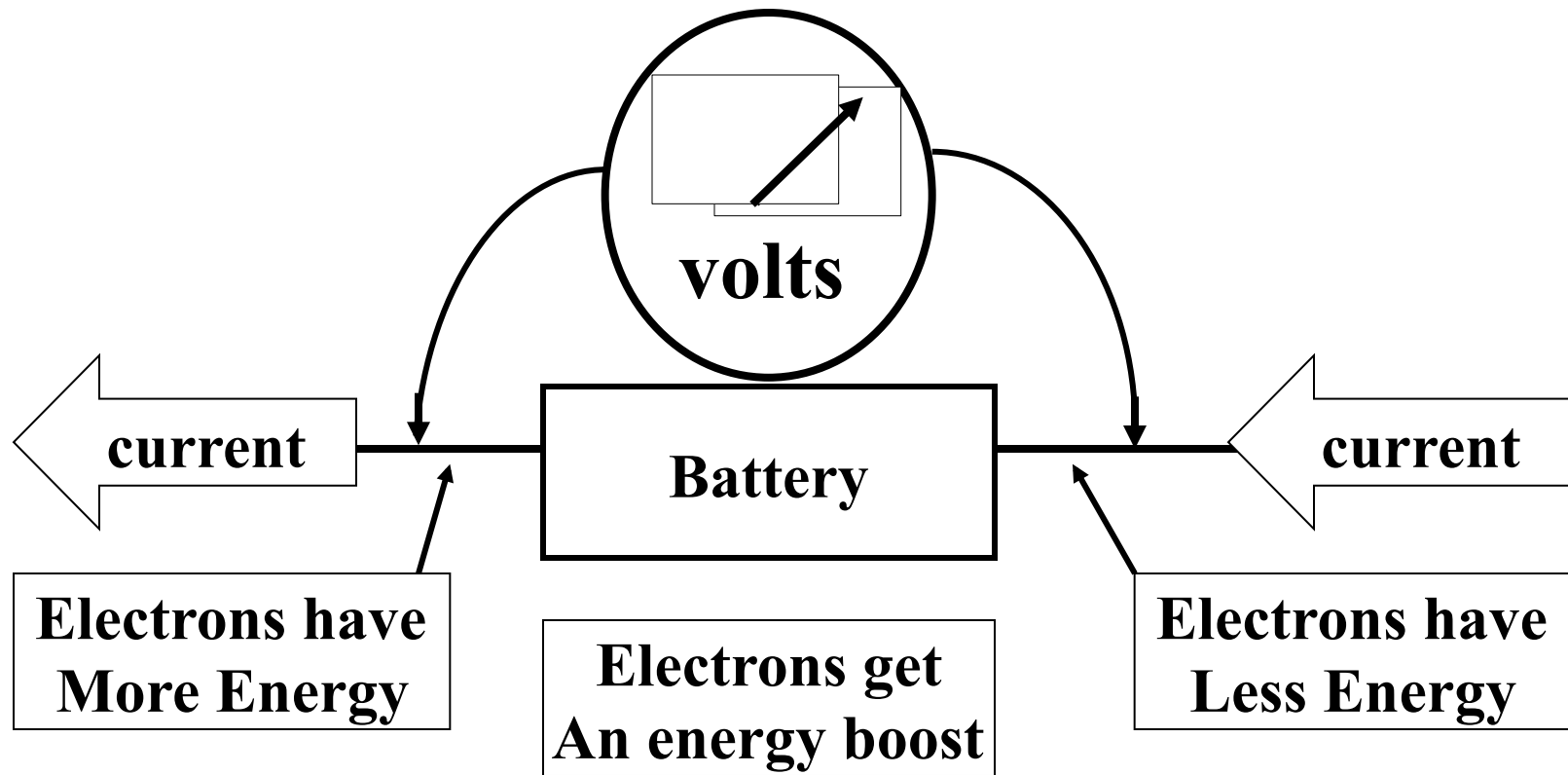

# Potential Drop Across a Resistor

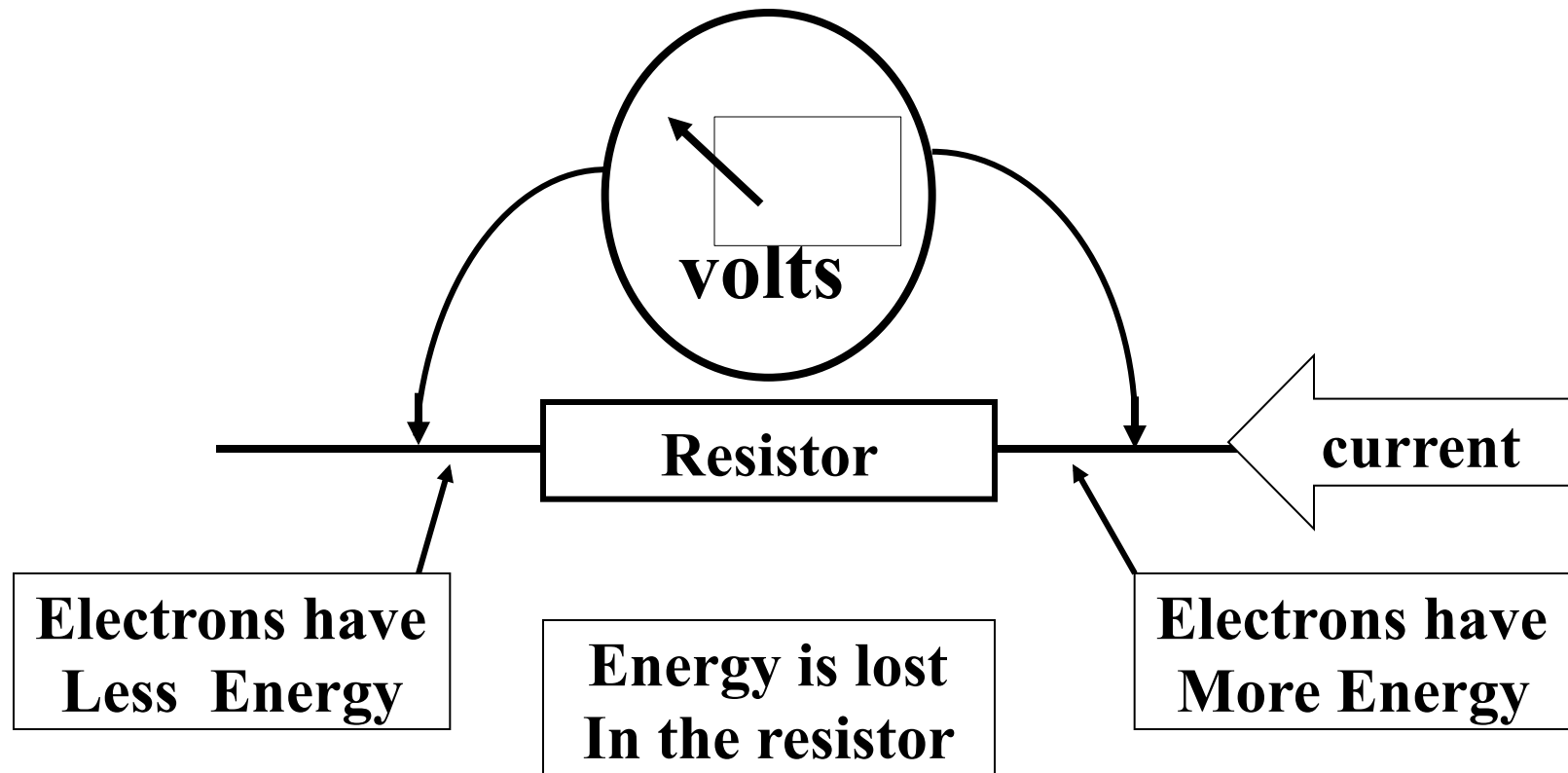

# **MEASUREABLE QUANTITIES THAT CAN BE OBTAINED FROM AN ELECTRICAL CIRCUIT**

**(1) VOLTAGE RISE – MEASURES THE ENERGY GIVEN TO ELECTRONS AS THEY LEAVE A VOLTAGE SOURCE. IT IS MEASURED IN VOLTS (+)**



**(2) VOLTAGE DROP – MEASURES THE ENERGY LOST BY TO ELECTRONS WHEN THEY LEAVE A RESISTANCE. IT IS MEASURED IN VOLTS (-)**

**(3) CURRENT – MEASURES THE FLOW RATE THROUGH A CONDUCTOR. IT IS MEASURED IN AMPERES (AMPS)**


**(4) RESISTANCE – MEASURES THE OPPOSITION TO CURRENT FLOW THROUGH A CONDUCTOR OR RESISTOR  
IT IS MEASURED IN OHMS (ITS SYMBOL IS OMEGA )**
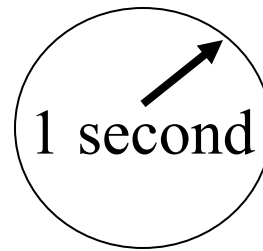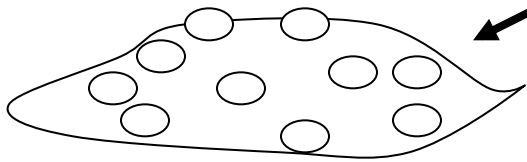
# ELECTRICAL QUANTITIES

$6.25 \times 10^{18}$  electrons  
1 coulomb



1 amp = 1 coul / sec

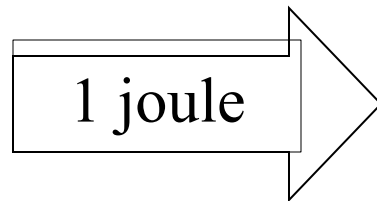


1 volt = 1 joule / coul


1 coulomb of charge



# Electrical Meters

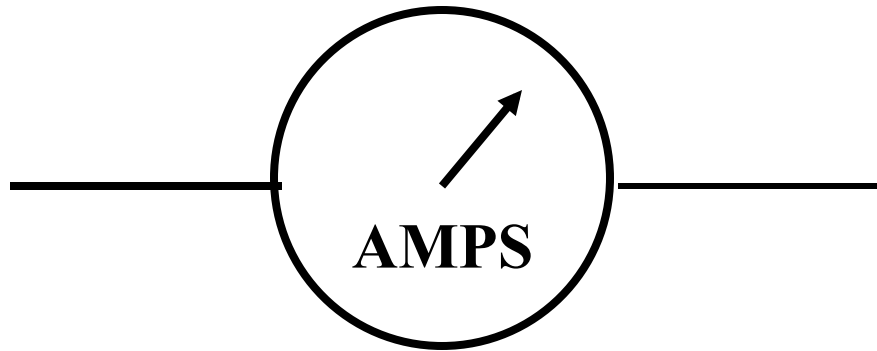

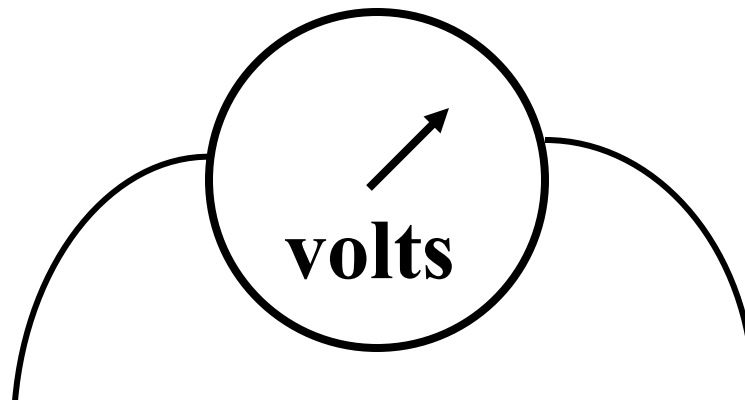**Ammeters measure current in amperes and are always wired in series in the circuit.**



**Voltmeters measure potential in volts and are always wired in parallel in the circuit.**

# *An actual Voltmeter*



# ***An Actual Ammeter***




# Electrical Symbols

battery



junction

 


wiring




terminal



voltmeter

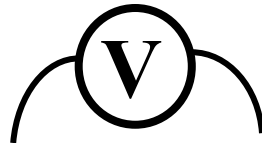


AC generator

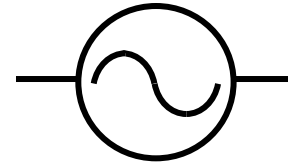

ammeter




Variable resistance

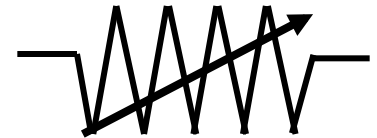


resistance



Variable capacitor

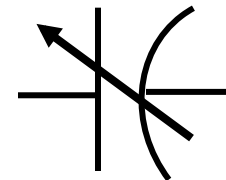

capacitor

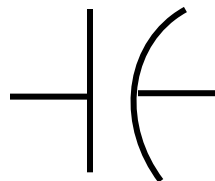

# **Relationships Among Electrical Quantities in a Circuit**

**Measure electrical quantities in an electrical  
Circuit are related to each other by:  
OHM' S LAW**

**OHM' S LAW says, if the source voltage remains constant,  
increasing the resistance in a circuit will cause a decrease  
in current flow in that circuit.**

**In mathematical terms it tells us that current flow is  
inversely proportional to resistance.**

**In equation form it says:  
Voltage (V) = Current (I) x Resistance (R)  
or  
V(in volts) = I (in amps) x R (in ohms)**

# Ohm's Law

$$V = IR$$

**Potential**  
In volts  
(joules / coul)


**Drop across a  
resistance**

**Current**  
In amperes  
(coul / second)

**Current passing  
Through the  
resistor**

**Resistance**  
In ohms  
(volts / amp)
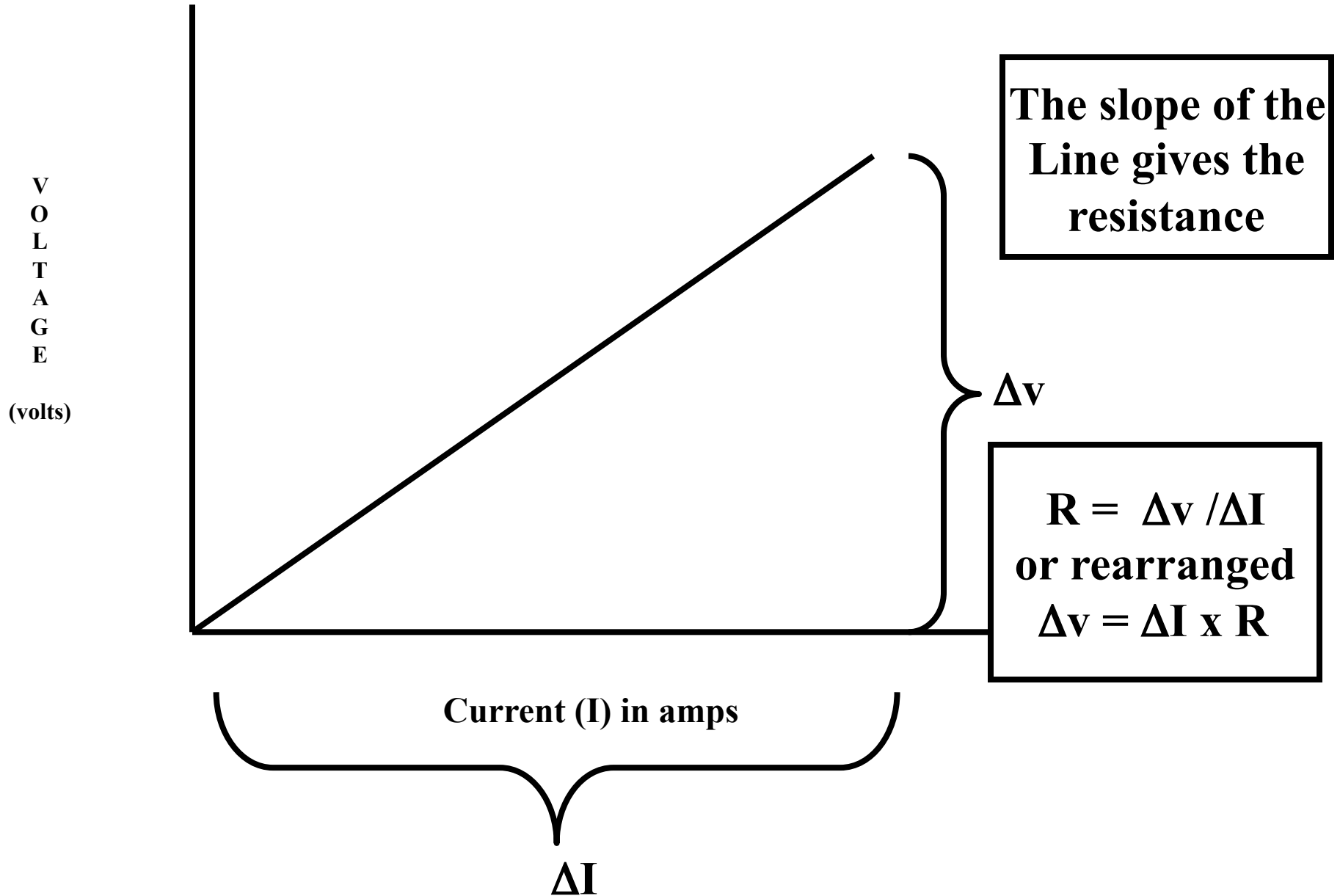
# Voltage vs Current for a Constant Resistance



# Voltage Sources and Internal Resistance

All voltage sources contain internal resistance, that is resistance that is part of the voltage producing device itself which cannot be eliminated.


The voltage that the device (battery for example) could produce if no internal resistance was present is called its EMF.

EMF stands for electromotive force – the force that moves the electrons.

The useable voltage which is available to the circuit after the internal resistance consumes its share of the EMF is called The terminal voltage.


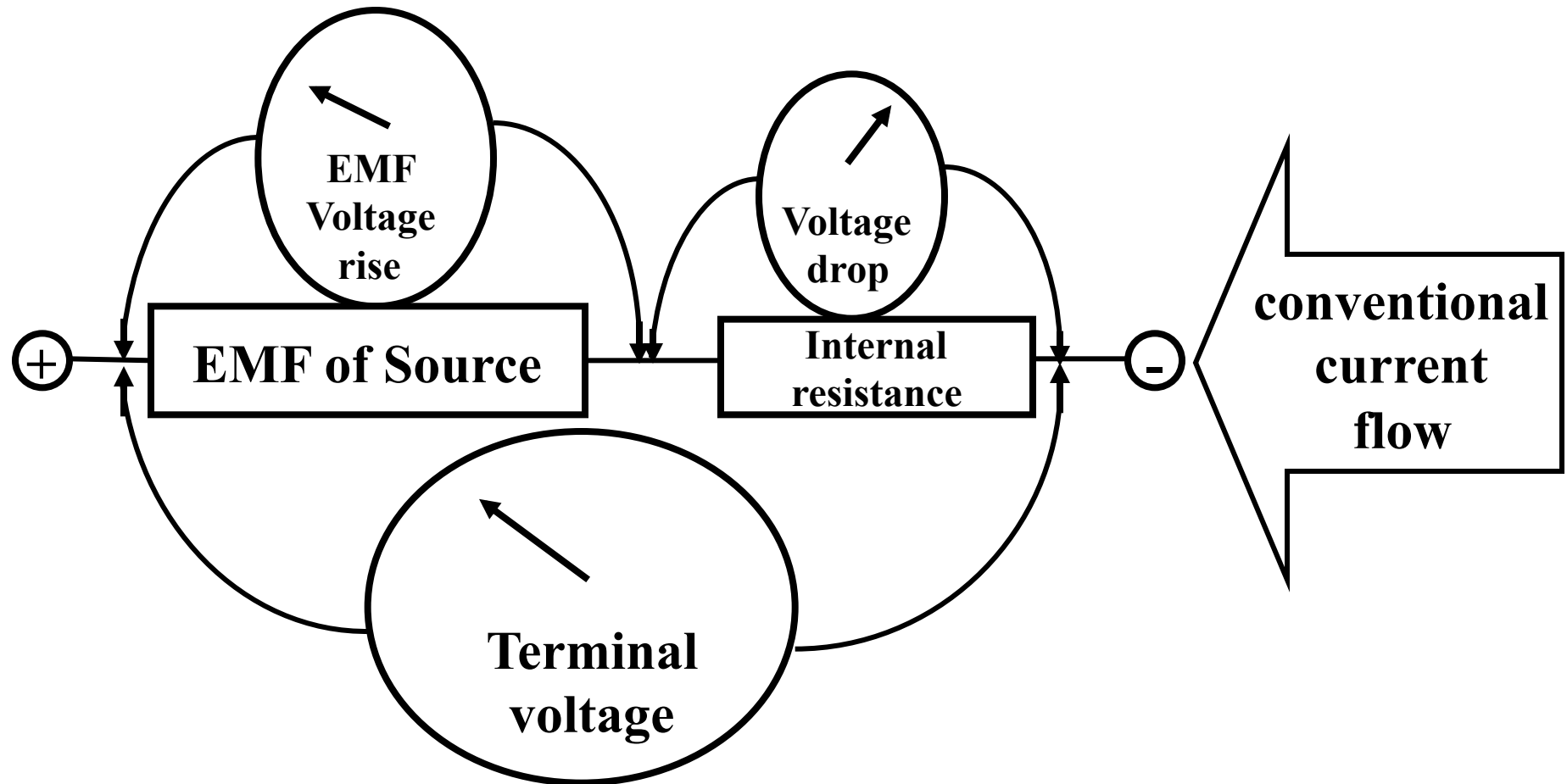
# Electromotive Force (EMF) and Terminal Voltage



# **terminal voltage = EMF (+) + Internal resistance loss (-)**

**Since voltage rise across a source or  
Voltage drop across a resistance can be  
Calculated by Ohm's Law**

$$V = IR$$

**And the above equation becomes**


$$V_{\text{terminal}} = \text{EMF} - I \times R_{\text{internal}}$$

**Note that if  $R_{\text{internal}}$  is very small then a large  
Percentage of the EMF is available to the circuit.**

**Also note that if  $I$ , the current is very large then  
a large percentage of the EMF is consumed within  
the battery itself which can cause overheating and failure.**


**This is generally the result of a short circuit.**

# Internal Resistance and EMF

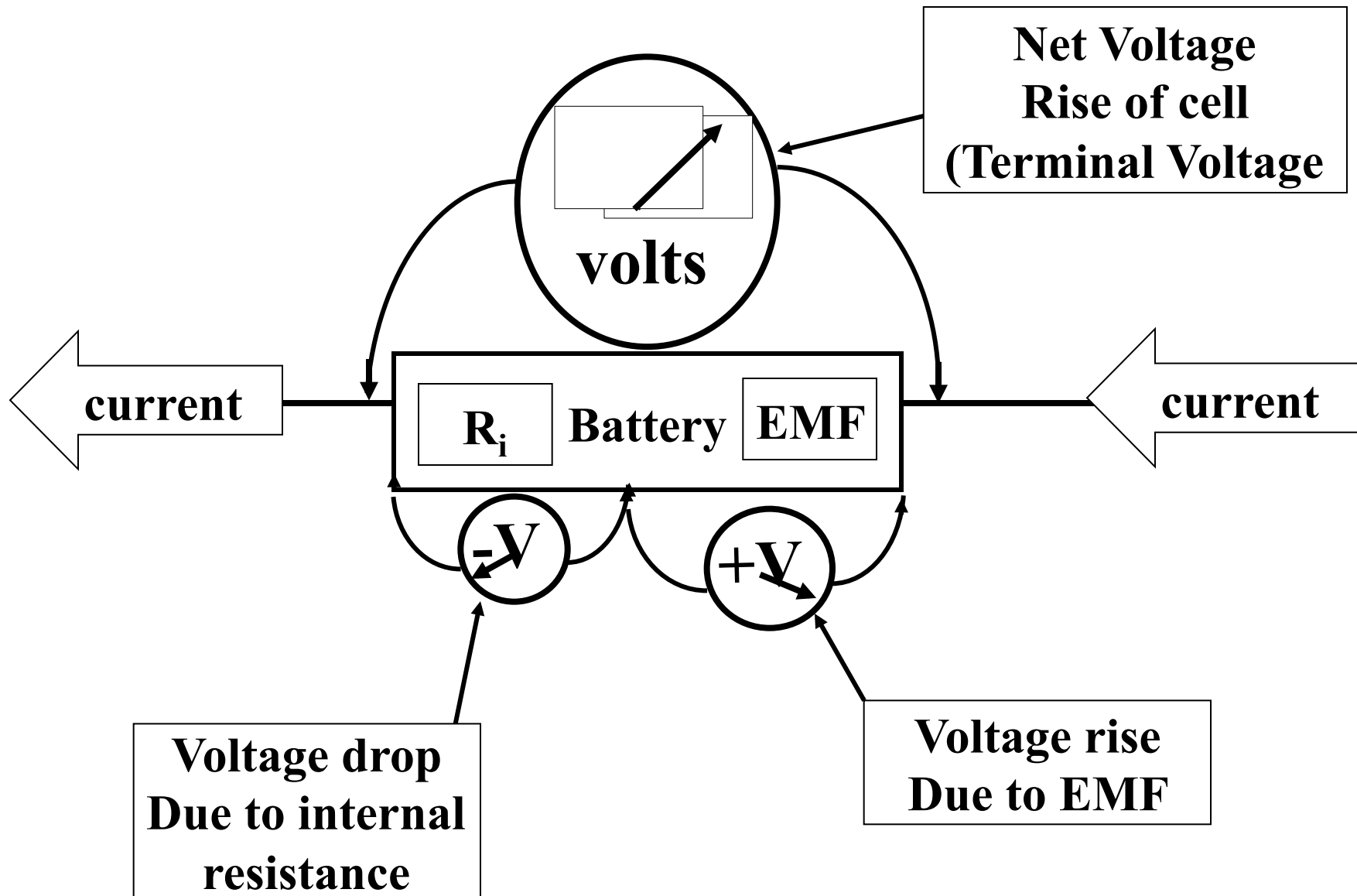

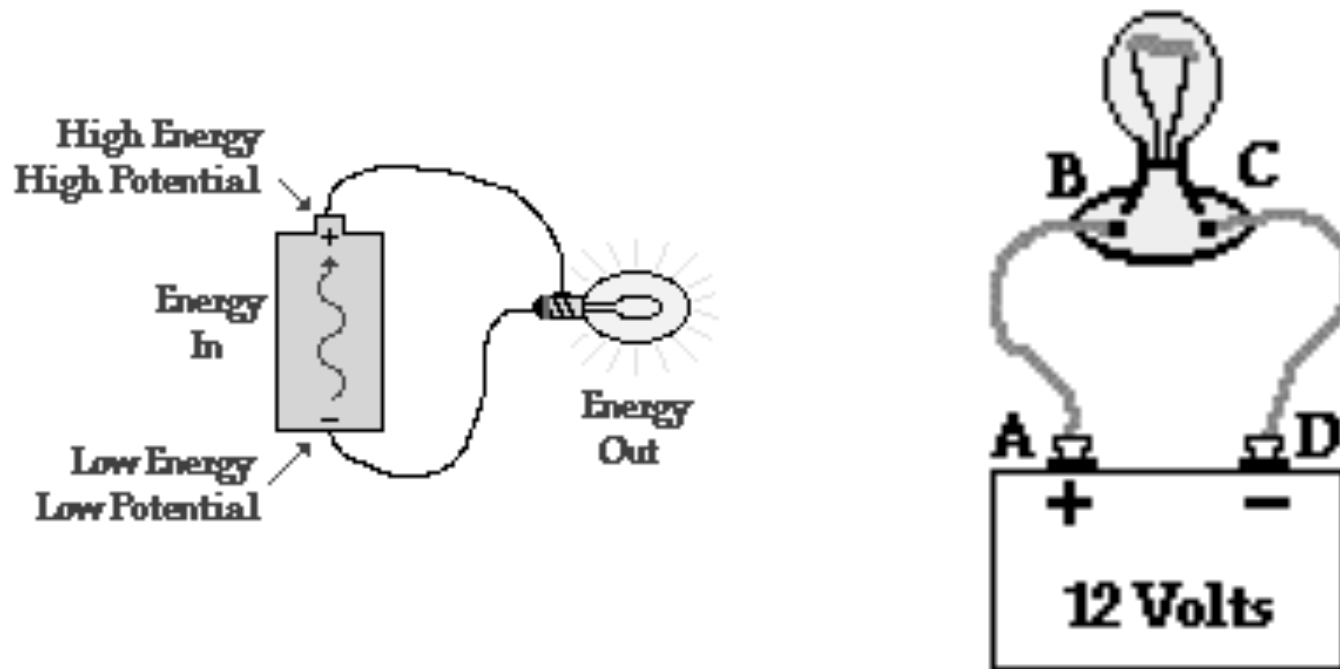
# Electric Circuit

Electric Circuit – a closed loop of electron flow.



# Circuit Symbols

## Symbols

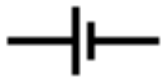

**Single Cell**



**Battery**



**Connecting wire**



**Resistor**




**Switch (open)**




**Switch (closed)**

**Drawing of Circuit**

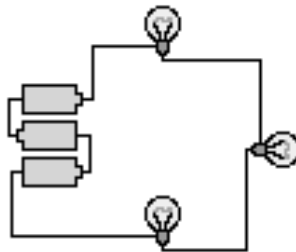


**Schematic Diagram of Circuit**

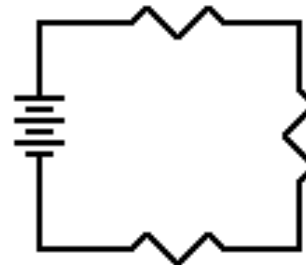


# Circuits

**Drawing of Circuit**

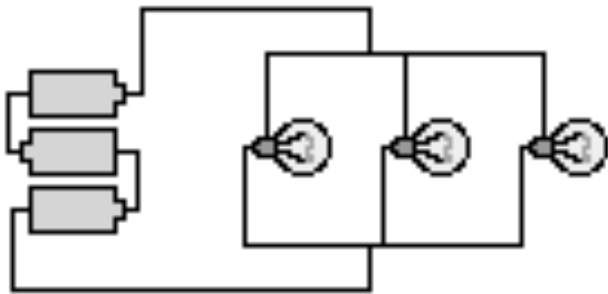

**Schematic Diagram of Circuit**

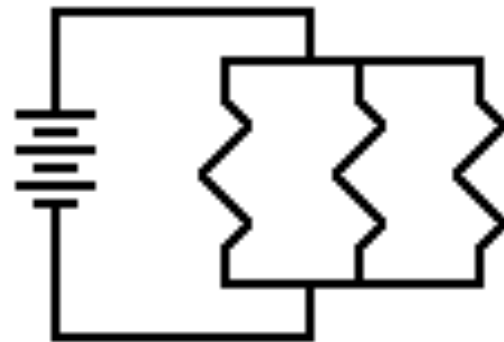

# Types of Circuits

Series

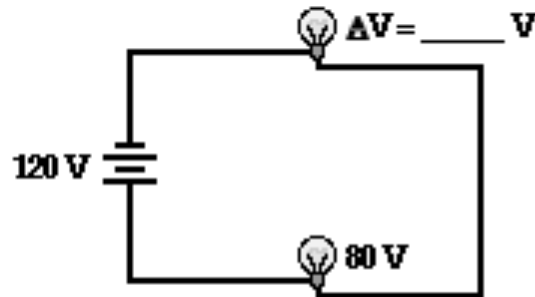


Diagram A


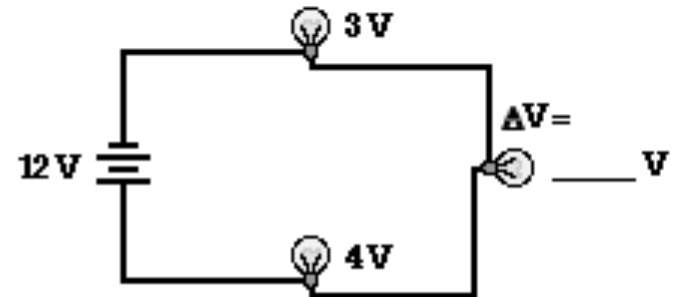
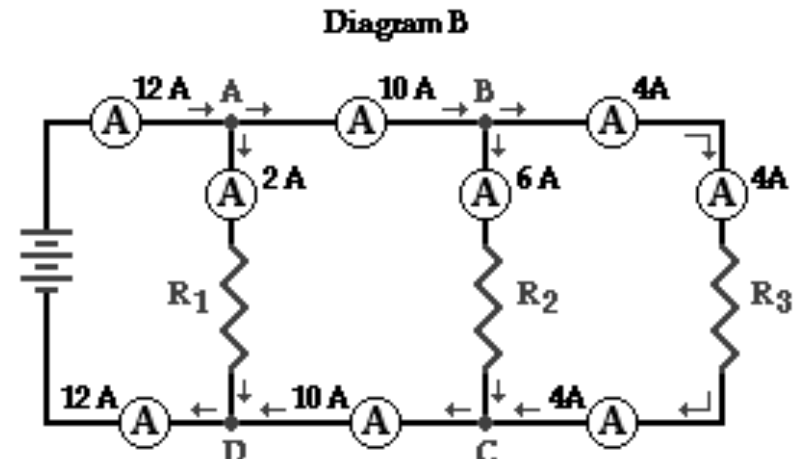


Diagram B

Parallel

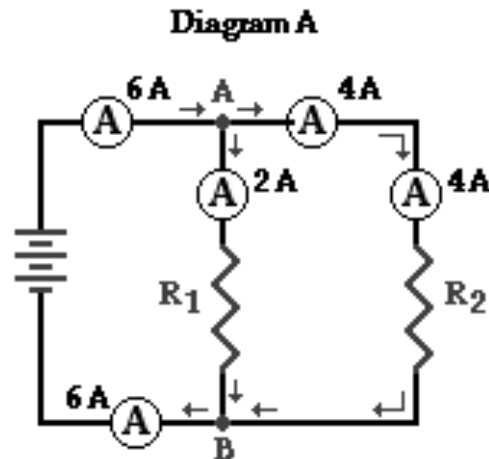

# Types of Circuits

## Combination

